

DSD LAB SEE Verilog Codes (Xilinx)

1.Code and simulate all Basic gates.


NOT Gate:

➤ *Verilog Code:*

```
module not_gate(a, y);  
    input a;  
    output y;  
    not G1(y,a);  
endmodule
```

➤ *Verilog Test Fixture : (Input combinations)*

1. a=0;
2. a=1;

 


OR Gate:

➤ *Verilog Code:*

```
module or_gate(a, b, y);  
    input a;  
    input b;  
    output y;  
    or G1(y,a,b);  
endmodule
```

➤ *Verilog Test Fixture : (Input combinations)*

 1. a=0;
b=0;
2. a=0;
b=1;
3. a=1;
b=0;
4. a=1;
b=1;




AND Gate:

➤ *Verilog Code:*

```
module and_gate(a, b, y);  
    input a;  
    input b;  
    output y;  
    and G1(y,a,b);  
endmodule
```

➤ *Verilog Test Fixture : (Input combinations)*

 1. a=0;
b=0;
2. a=0;
b=1;
3. a=1;
b=0;
4. a=1;
b=1;




XOR Gate:

➤ Verilog Code:

```
module xor_gate(a, b, y);  
    input a;  
    input b;  
    output y;  
    xor G1(y,a,b);  
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

 1. a=0;
b=0;
2. a=0;
b=1;
3. a=1;
b=0;
4. a=1;
b=1;




NAND Gate:

➤ Verilog Code:

```
module nand_gate(a, b, y);  
    input a;  
    input b;  
    output y;  
    nand G1(y,a,b);  
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

 1. a=0;
b=0;
2. a=0;
b=1;
3. a=1;
b=0;
4. a=1;
b=1;




NOR Gate:

➤ Verilog Code:

```
module nor_gate(a, b, y);  
    input a;  
    input b;  
    output y;  
    nor G1(y,a,b);  
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

 5. a=0;
b=0;
6. a=0;
b=1;
7. a=1;
b=0;
8. a=1;
b=1;




2. Simulation of 4:1 multiplexer using data flow model.

➤ Verilog Code:

```
module mux4to1(d0, d1, d2, d3, a, b, y);  
    input d0;  
    input d1;  
    input d2;  
    input d3;  
    input a;  
    input b;  
    output y;  
  
    assign  
y=(~a&~b&d0)|(~a&b&d1)|(a&~b&d2)|(a&b&d3);  
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

 1. d0 = 0; d1 = 0; d2 = 0; d3 = 0; a = 0; b = 0;
2. d0 = 1; d1 = 0; d2 = 0; d3 = 0; a = 0; b = 0;
3. d0 = 0; d1 = 0; d2 = 0; d3 = 0; a = 0; b = 1;
4. d0 = 0; d1 = 1; d2 = 0; d3 = 0; a = 0; b = 1;
5. d0 = 0; d1 = 0; d2 = 0; d3 = 0; a = 1; b = 0;
6. d0 = 0; d1 = 0; d2 = 1; d3 = 0; a = 1; b = 0;
7. d0 = 0; d1 = 0; d2 = 0; d3 = 0; a = 1; b = 1;
8. d0 = 0; d1 = 0; d2 = 0; d3 = 1; a = 1; b = 1;




3. Simulation of 8:1 multiplexer.

➤ Verilog Code:

```
module mux8to1(d0, d1, d2, d3, d4, d5, d6, d7, a, b, c, y);  
    input d0;  
    input d1;  
    input d2;  
    input d3;  
    input d4;  
    input d5;  
    input d6;  
    input d7;  
    input a;  
    input b;  
    input c;  
    output y;  
    reg y;  
  
    always @(a or b or c or d0 or d1 or d2 or d3 or d4 or d5 or d6 or d7)  
    case({a,b,c})  
        0:y=d0;  
        1:y=d1;  
        2:y=d2;  
        3:y=d3;  
        4:y=d4;  
        5:y=d5;  
        6:y=d6;  
        7:y=d7;  
  
    endcase  
endmodule
```

➤ *Verilog Test Fixture : (Input combinations)*

 1. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 0; c=0;
2. d0 = 1; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 0; c=0;
3. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 0; c=1;
4. d0 = 0; d1 = 1; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 0; c=1;
5. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 1; c=0;
6. d0 = 0; d1 = 0; d2 = 1; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 1; c=0;
7. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 1; c=1;
8. d0 = 0; d1 = 0; d2 = 0; d3 = 1; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 0; b = 1; c=1;
9. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 1; b = 0; c=0;
10. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 1; d5 = 0; d6 = 0; d7 = 0; a = 1; b = 0; c=0;
11. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 1; b = 0; c=1;
12. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 1; d6 = 0; d7 = 0; a = 1; b = 0; c=1;
13. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 1; b = 1; c=0;
14. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 1; d7 = 0; a = 1; b = 1; c=0;
15. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 0; a = 1; b = 1; c=1;
16. d0 = 0; d1 = 0; d2 = 0; d3 = 0; d4 = 0; d5 = 0; d6 = 0; d7 = 1; a = 1; b = 1; c=1;




4.Simulation of Half adder using Data Flow model.

➤ *Verilog Code:*

```
module half_adder(a, b, sum, carry);
    input a;
    input b;
    output sum;
    output carry;
    assign sum=a^b;
    assign carry=a&b;
endmodule
```

➤ *Verilog Test Fixture : (Input combinations)*

 1. a=0;
 b=0;
2. a=0;
 b=1;
3. a=1;
 b=0;
4. a=1;
 b=0;




5. Simulation of Half adder using Behavioral model.

➤ Verilog Code:

```
module ha(a, b, sum, carry);
    input a;
    input b;
    output sum;
    output carry;
    reg sum;
    reg carry;
    always @(a or b)
        case({a,b})
            0: begin
                sum=0; carry=0;
            end
            1: begin
                sum=1; carry=0;
            end
            2: begin
                sum=1; carry=0;
            end
            3: begin
                sum=0; carry=1;
            end
        endcase
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

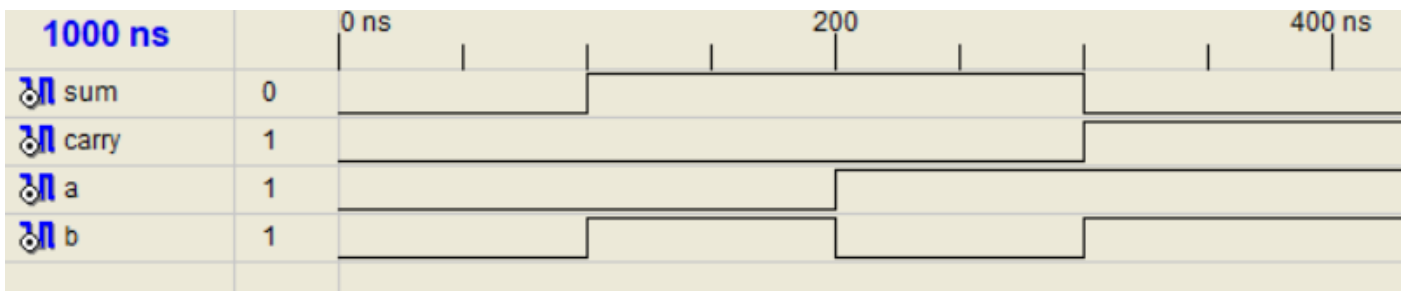1. a=0;
b=0;
2. a=0;
b=1;
3. a=1;
b=0;
4. a=1;
b=0;



6. Simulation of Full adder.

➤ Verilog Code:

```
module full_adder(a, b, c, sum, carry);
    input a;
    input b;
    input c;
    output sum;
    output carry;
    reg sum;
    reg carry;
    always @(a or b or c)
        case({a,b,c})
            0: begin
                sum=0; carry=0;
            end
            1: begin
                sum=0; carry=0;
            end
            2: begin
                sum=0; carry=0;
            end
            3: begin
                sum=0; carry=0;
            end
            4: begin
                sum=0; carry=0;
            end
            5: begin
                sum=0; carry=0;
            end
            6: begin
                sum=0; carry=0;
            end
            7: begin
                sum=0; carry=0;
            end
            8: begin
                sum=0; carry=0;
            end
            9: begin
                sum=0; carry=0;
            end
            10: begin
                sum=0; carry=0;
            end
            11: begin
                sum=0; carry=0;
            end
            12: begin
                sum=0; carry=0;
            end
            13: begin
                sum=0; carry=0;
            end
            14: begin
                sum=0; carry=0;
            end
            15: begin
                sum=0; carry=0;
            end
        endcase
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

1. a=0;
b=0;
c=0;
2. a=0;
b=0;
c=1;
3. a=0;
b=1;
c=0;
4. a=0;
b=1;
c=1;
5. a=1;
b=0;
c=0;

```


1: begin
    sum=1; carry=0;
end
2: begin
    sum=1; carry=0;
end
3: begin
    sum=0; carry=1;
end
4: begin
    sum=1; carry=0;
end
5: begin
    sum=0; carry=1;
end
6: begin
    sum=0; carry=1;
end
7: begin
    sum=1; carry=1;
end
endcase
endmodule

```

```

6. a=1;
   b=0;
   c=1;
7. a=1;
   b=1;
   c=1;
8. a=1;
   b=1;
   c=1;

```

 

7.Simulation of 1:8 demultiplexer.

➤ Verilog Code:

```

module demux1to8(a, b, c, D, y0, y1, y2, y3, y4, y5, y6, y7);
    input a;
    input b;
    input c;
    input D;
    output y0,y1,y2,y3,y4,y5,y6,y7;
    reg y0,y1,y2,y3,y4,y5,y6,y7;
    always @(a or b or c or D)
    case({a,b,c})
        0:begin
            y0=D; y1=0; y2=0; y3=0; y4=0; y5=0; y6=0; y7=0;
        end
        1:begin
            y0=0; y1=D; y2=0; y3=0; y4=0; y5=0; y6=0; y7=0;
        end
    endcase
endmodule

```


➤ Verilog Test Fixture : (Input combinations)

1. a=0; b=0; c=0; d=0;
2. a=0; b=0; c=0; d=1;
3. a=0; b=0; c=1; d=0;
4. a=0; b=0; c=1; d=1;
5. a=0; b=1; c=0; d=0;
6. a=0; b=1; c=0; d=1;
7. a=0; b=1; c=1; d=0;
8. a=0; b=1; c=1; d=1;
9. a=1; b=0; c=0; d=0;
10. a=1; b=0; c=0; d=1;
11. a=1; b=0; c=1; d=0;
12. a=1; b=0; c=1; d=1;
13. a=1; b=1; c=0; d=0;
14. a=1; b=1; c=0; d=1;
15. a=1; b=1; c=1; d=0;
16. a=1; b=1; c=1; d=1;

```

2:begin
    y0=0; y1=0; y2=D; y3=0; y4=0; y5=0; y6=0; y7=0;
end
3:begin
    y0=0; y1=0; y2=0; y3=D; y4=0; y5=0; y6=0; y7=0;
end
4:begin
    y0=0; y1=0; y2=0; y3=0; y4=D; y5=0; y6=0; y7=0;
end
5:begin
    y0=0; y1=0; y2=0; y3=0; y4=0; y5=D; y6=0; y7=0;
end
6:begin
    y0=0; y1=0; y2=0; y3=0; y4=0; y5=0; y6=D; y7=0;
end
7:begin
    y0=0; y1=0; y2=0; y3=0; y4=0; y5=0; y6=0; y7=D;
end
endcase
endmodule

```

 

8.Simulation of 3:8 decoder.

➤ Verilog Code:

```

module decoder3to8(a, b, c, y0, y1, y2, y3, y4, y5, y6, y7);
    input a;
    input b;
    input c;
    output y0,y1,y2,y3,y4,y5,y6,y7;
    reg y0,y1,y2,y3,y4,y5,y6,y7;
    always @(a or b or c)
        case({a,b,c})
            0: begin
                y0=1; y1=0; y2=0; y3=0; y4=0; y5=0; y6=0; y7=0;
            end
            1: begin
                y0=0; y1=1; y2=0; y3=0; y4=0; y5=0; y6=0; y7=0;
            end

```

➤ Verilog Test Fixture : (Input combinations)

1. a=0;
b=0;
c=0;
2. a=0;
b=0;
c=1;
3. a=0;
b=1;
c=0;
4. a=0;
b=1;
c=1;
5. a=1;
b=0;
c=0;

```


2: begin
    y0=0; y1=0; y2=1; y3=0; y4=0; y5=0; y6=0; y7=0;
end
3: begin
    y0=0; y1=0; y2=0; y3=1; y4=0; y5=0; y6=0; y7=0;
end
4: begin
    y0=0; y1=0; y2=0; y3=0; y4=1; y5=0; y6=0; y7=0;
end
5: begin
    y0=0; y1=0; y2=0; y3=0; y4=0; y5=1; y6=0; y7=0;
end
6: begin
    y0=0; y1=0; y2=0; y3=0; y4=0; y5=0; y6=1; y7=0;
end
7: begin
    y0=0; y1=0; y2=0; y3=0; y4=0; y5=0; y6=0; y7=1;
end
endcase
endmodule

```

```

6. a=1;
   b=0;
   c=1;
7. a=1;
   b=1;
   c=1;
8. a=1;
   b=1;
   c=1;

```

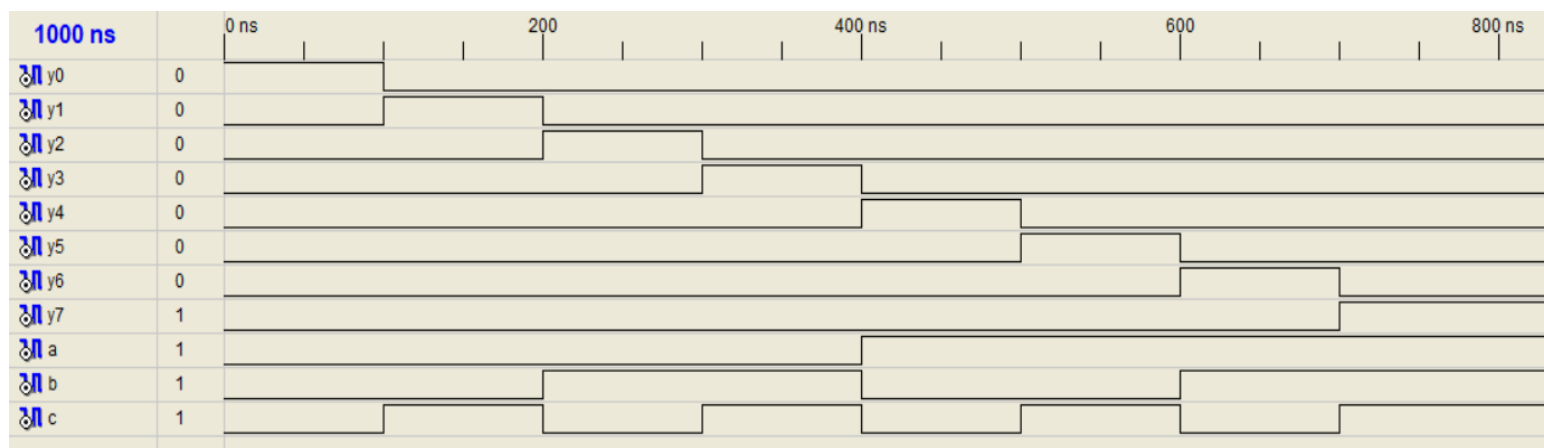

9.Simulation of flip flops : i)D flip flop ii)RS flip flop

i)a.Gated D Flip Flop:

➤ Verilog Code:


```

module gated_D_FF(D, EN, Q);
    input D;
    input EN;
    output Q;
    reg Q;
    always @(D or EN)
    if(EN)
        Q=D;
endmodule

```

➤ Verilog Test Fixture : (Input combinations)

 1. D=0; EN=1;
2. D=1; EN=1;
3. D=0; EN=0;
4. D=0; EN=1;
5. D=1; EN=0;
6. D=1; EN=1;




i)b.Edge Triggered D Flip Flop:

➤ Verilog Code:

```
module edge_triggered_D_FF(D, CLK, Q);  
    input D;  
    input CLK;  
    output Q;  
    reg Q;  
    always @(posedge CLK)  
        Q=D;  
  
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

 1. D=0; CLK=0;
2. D=0; CLK=1;
3. D=1; CLK=0;
4. D=1; CLK=1;
5. D=0; CLK=0;
6. D=0; CLK=1;
7. D=1; CLK=0;
8. D=1; CLK=1;




ii)a.Gated RS Flip Flop:

➤ Verilog Code:

```
module gated_RS_FF(R,S, EN, Q);  
    input R;  
    input S;  
    input EN;  
    output Q;  
    reg Q;  
    always @(R or S or EN)  
        if(EN)  
            Q=S|(~R&Q);  
  
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

 1. R=1; S=0; EN=1;
2. R=0; S=0; EN=1;
3. R=0; S=1; EN=1;
4. R=0; S=0; EN=1;
5. R=1; S=0; EN=0;
6. R=1; S=0; EN=1;




ii)b.Edge Triggered RS Flip Flop:

➤ Verilog Code:

```
module edge_triggered_RS_FF(R,S, CLK, Q);  
    input R;  
    input S;  
    input CLK;  
    output Q;  
    reg Q;  
    always @(posedge CLK)  
        Q=S|(~R&Q);  
  
endmodule
```

➤ Verilog Test Fixture : (Input combinations)

 1. R=1; S=0; CLK=0;
2. R=1; S=0; CLK=1;
3. R=0; S=1; CLK=0;
4. R=0; S=1; CLK=1;
5. R=0; S=0; CLK=0;
6. R=0; S=0; CLK=1;
7. R=1; S=0; CLK=0;
8. R=1; S=0; CLK=1;
9. R=0; S=1; CLK=0;



10. Simulation of Ring counter

➤ *Verilog Code:*


```

module ring_counter(CLK, Q, R, S, T);
    input CLK;
    output Q,R,S,T;
    reg Q,R,S,T;
        initial
            begin
                Q=1; R=0; S=0; T=0;
            end
        always @(posedge CLK)
            begin
                Q<=T; R<=Q; S<=R; T<=S;
            end
    endmodule

```

- *Verilog Test Fixture : (Input combinations)*

 1. CLK=0;
2. CLK=1;
3. CLK=0;
4. CLK=1;
5. CLK=0;
6. CLK=1;
7. CLK=0;
8. CLK=1;
9. CLK=0;
10. CLK=1;
11. CLK=0;
12. CLK=1;
13. CLK=0;
14. CLK=1;
15. CLK=0;
16. CLK=1;
17. CLK=0;



11. Simulation of Johnson counter

➤ *Verilog Code:*

```

module johnson_counter(CLK, Q, R, S, T);
    input CLK;
    output Q,R,S,T;
    reg Q,R,S,T;
        initial
            begin
                Q=0; R=0; S=0; T=0;
            end
        always @(posedge CLK)
            begin
                Q<=~T; R<=Q; S<=R; T<=S;
            end
    endmodule

```

- *Verilog Test Fixture : (Input combinations)*

1. CLK=0;
2. CLK=1;
3. CLK=0;
4. CLK=1;
5. CLK=0;
6. CLK=1;
7. CLK=0;
8. CLK=1;
9. CLK=0;
10. CLK=1;
11. CLK=0;
12. CLK=1;
13. CLK=0;
14. CLK=1;
15. CLK=0;
16. CLK=1;
17. CLK=0;

